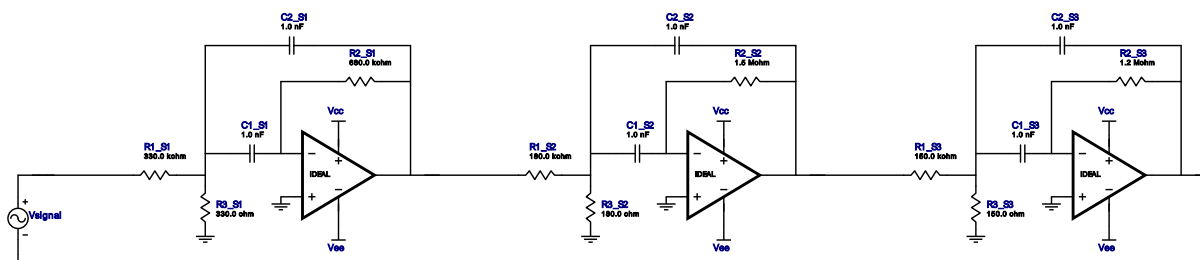


Filter Design Report

Design : Bandpass Filter - 6th order Chebyshev
Design ID: 29






Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty
1.	A1_S1	Texas Instruments Inc.	IDEAL	GbwTyp= 0MHz VccMax= 0V VccMin= 0V	1
2.	A1_S2	Texas Instruments Inc.	IDEAL	GbwTyp= 0MHz VccMax= 0V VccMin= 0V	1
3.	A1_S3	Texas Instruments Inc.	IDEAL	GbwTyp= 0MHz VccMax= 0V VccMin= 0V	1
4.	C1_S1	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
5.	C1_S2	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
6.	C1_S3	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
7.	C2_S1	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
8.	C2_S2	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
9.	C2_S3	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
10.	R1_S1	Generic	Ideal	Res= 330000.0ohm Tolerance= 10%	1
11.	R1_S2	Generic	Ideal	Res= 180000.0ohm Tolerance= 10%	1
12.	R1_S3	Generic	Ideal	Res= 150000.0ohm Tolerance= 10%	1
13.	R2_S1	Generic	Ideal	Res= 680000.0ohm Tolerance= 10%	1
14.	R2_S2	Generic	Ideal	Res= 1500000.0ohm Tolerance= 10%	1
15.	R2_S3	Generic	Ideal	Res= 1200000.0ohm Tolerance= 10%	1
16.	R3_S1	Generic	Ideal	Res= 330.0ohm Tolerance= 10%	1

#	Name	Manufacturer	Part Number	Properties	Qty
17.	R3_S2	Generic	Ideal	Res= 180.0ohm Tolerance= 10%	1
18.	R3_S3	Generic	Ideal	Res= 150.0ohm Tolerance= 10%	1

Sensitivity Analysis

#	Name	Series	Tolerance
1.	Cap	E6	20%
2.	Res	E12	10%

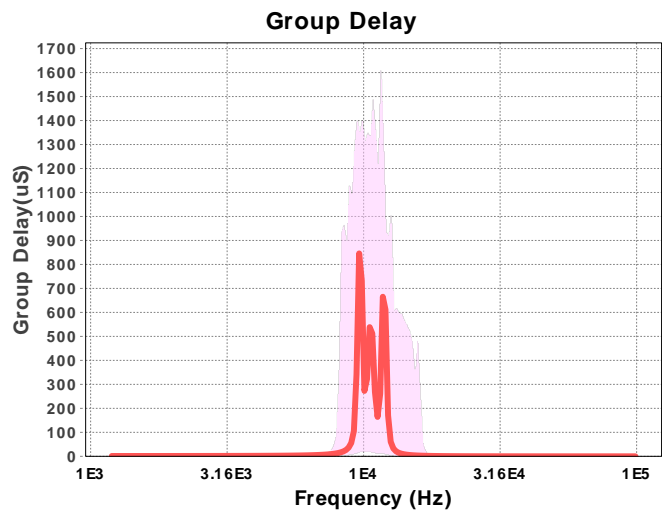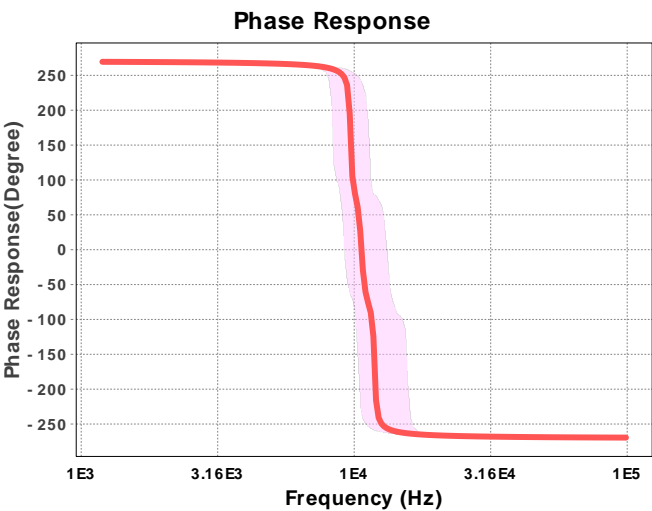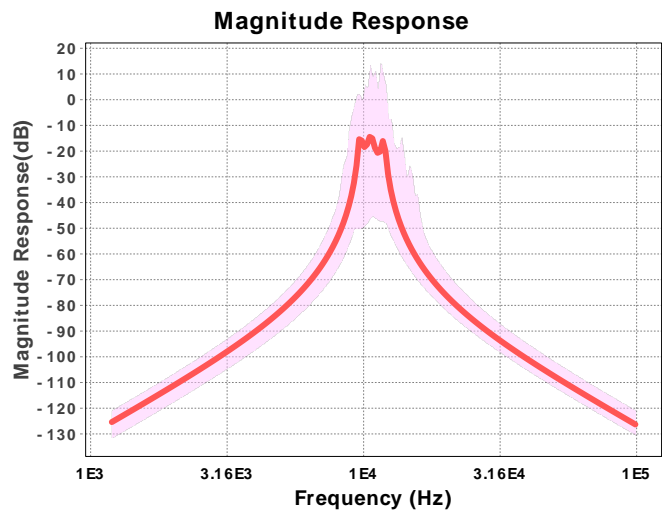

Design Inputs


#	Name	Value	Description
1.	FilterType	bandpass	
2.	FilterResponse	Chebyshev	
3.	FilterOrder	6.0	
4.	FilterTopology	Multiple Feedback	
5.	NumberOfStages	3.0	
6.	CenterFrequency	11.0 k	
7.	StopbandAttenuation	-66.108	
8.	PassbandBandwidth	1,000.0	
9.	StopbandBandwidth	10.0 k	
10.	Gain	1.0	
11.	DualSupply	+/-5.00 V	Power supply(s) to active chips
12.	ResistorTolerance	E12	Resistor series - 10% Passive resistor tolerance
13.	CapacitorTolerance	E6	Capacitor series - 20% Passive capacitor tolerance

Design Assistance

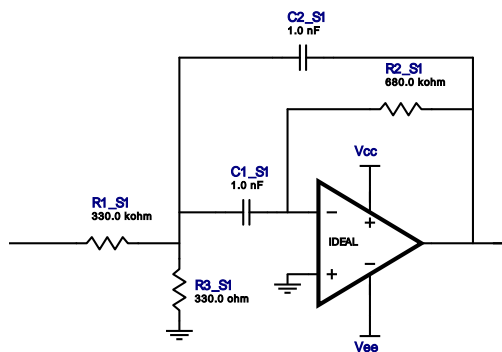1. **IDEAL** Product Folder : <http://www.ti.com/product/IDEAL> : contains the data sheet and other resources.

Filter Stage :1

Cutoff Frequency 10.63 kHz
 Min GBW Req'd 24.485 MHz
 Stage Gain 1.03 V/V
 Stage Q 22.708
 Stage Topology Multiple Feedback




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty
1.	A1_S1	Texas Instruments Inc.	IDEAL	GbwTyp= 0MHz VccMax= 0V VccMin= 0V	1
2.	C1_S1	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
3.	C2_S1	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
4.	R1_S1	Generic	Ideal	Res= 330000.0ohm Tolerance= 10%	1
5.	R2_S1	Generic	Ideal	Res= 680000.0ohm Tolerance= 10%	1
6.	R3_S1	Generic	Ideal	Res= 330.0ohm Tolerance= 10%	1

Filter Stage :2

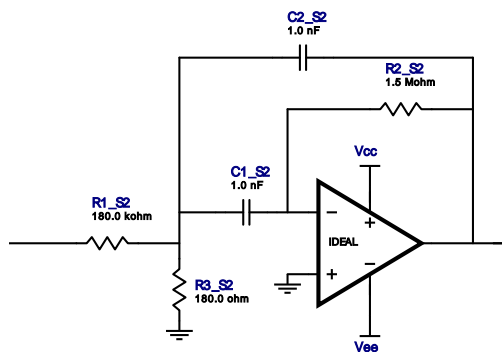Cutoff Frequency 9.691 kHz
 Min GBW Req'd 189.492 MHz
 Stage Gain 4.167 V/V
 Stage Q 45.666
 Stage Topology Multiple Feedback




Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty
1.	A1_S2	Texas Instruments Inc.	IDEAL	GbwTyp= 0MHz VccMax= 0V VccMin= 0V	1
2.	C1_S2	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
3.	C2_S2	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
4.	R1_S2	Generic	Ideal	Res= 180000.0ohm Tolerance= 10%	1
5.	R2_S2	Generic	Ideal	Res= 1500000.0ohm Tolerance= 10%	1
6.	R3_S2	Generic	Ideal	Res= 180.0ohm Tolerance= 10%	1

Filter Stage :3

Cutoff Frequency	11.869 kHz
Min GBW Req'd	206.88 MHz
Stage Gain	4.0 V/V
Stage Q	44.744
Stage Topology	Multiple Feedback

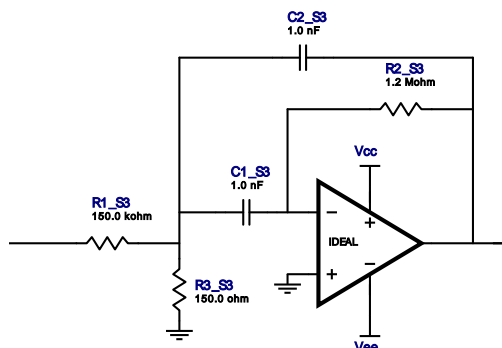

Electrical BOM

#	Name	Manufacturer	Part Number	Properties	Qty
1.	A1_S3	Texas Instruments Inc.	IDEAL	GbwTyp= 0MHz VccMax= 0V VccMin= 0V	1
2.	C1_S3	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
3.	C2_S3	Generic	Ideal	Cap= 1.0 nF Tolerance= 20.0 %	1
4.	R1_S3	Generic	Ideal	Res= 150000.0ohm Tolerance= 10%	1
5.	R2_S3	Generic	Ideal	Res= 1200000.0ohm Tolerance= 10%	1
6.	R3_S3	Generic	Ideal	Res= 150.0ohm Tolerance= 10%	1

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.